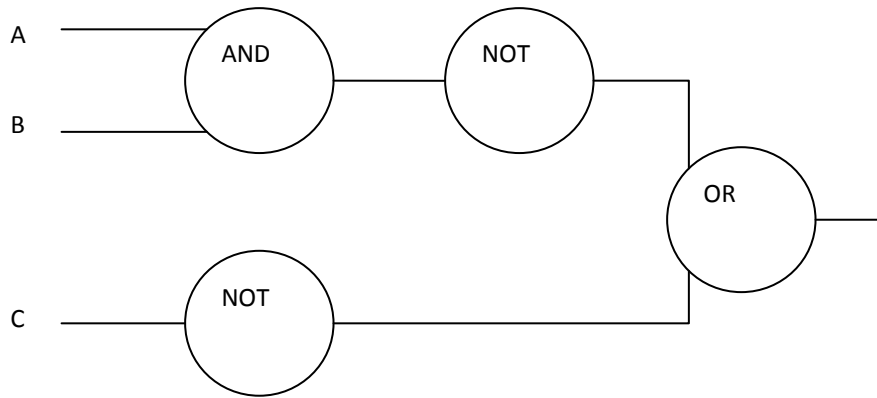


Handout 05 – Logic Circuits

1. What is the purpose of combining logic gates? (3)
2. Explain what truth tables are and why are these used. (3)
3. Draw the three basic logic gates and their respective truth tables. (6)
4. Draw the truth table for the following logic circuit. (5)



5. Draw the truth table for the following logic circuit. (5)

